

Jezik VHDL

N. Zimic

11-1

Modeliranje sistemov

- Jezik VHDL je namenjen opisovanju digitalnih vezij
- Razlogi:
 - vedno bolj zahtevni sistemi,
 - dokumentacija,
 - testiranje z uporabo simulacije,
 - formalno preverjanje,
 - sinteza.

N. Zimic

11-2

Modeliranje sistemov (nad.)

- Namen:
 - hitrejše načrtovanje vezij,
 - cenejše načrtovanje vezij,
 - zmanjšanje števila napak pri načrtovanju.


N. Zimic

11-3

Opis stukture

- Digitalni gradnik lahko opišemo:
 - z vhodi in izhodi,
 - z električnimi značilnostmi vhodov in izhodov.
- Primer VHDL gradnika (*entity*) z vhodoma *A* in *B* ter izhodom *Y*.

$$Y = F(A, B)$$

 


N. Zimic

11-4

Opis stukture (nad.)

 - Gradnik/enetiteto (*entity*) lahko sestavlja več gradnikov:



N. Zimic

11-5


Opis stukture (nad.)

- Vsak gradnik, ki je del večjega gradnika je slika/primer (*instance*) osnovnega gradnika.
- Na prejšnji projekciji je predstavljen primer, kako je gradnik F sestavljen iz gradnikov G, H, I.
- Gradniki so med seboj povezani s signali.

N. Zimic

11-6

Gradniki VHDL

 

N. Zimic

11-7

Gradniki VHDL (nad.)

- Deklaracija entitete določa priključke entitete
- Telo entitete določa logično funkcijo entitete
- Deklaracija konfiguracije določa povezavo entitete z določeno arhitekturo
- Deklaracija knjižnice povezuje elemente
- Telo knjižnice vsebuje elemente iz deklaracije

N. Zimic


11-8

Deklaracija entitete

```
library ieee;
use ieee.std_logic_1164.all ; ← Podatki o knjižnici

entity Adder is
port ( A, B : in std_ulogic_vector(3 downto 0);
      Cin : in std_ulogic;
      Sum : out std_ulogic_vector(3 downto 0);
      Cout : out std_ulogic);
end Adder; ← Ime entitete
```

 Ime priključka Način delovanja priključka Tip priključka




N. Zimic


11-9

Način delovanja priključka


Način out

 


Način buffer

 

Način in

 

Način inout

 

N. Zimic

11-10

Opis arhitekture

Deklaracija priključka

```
entity Adder is  
end Adder;
```

Ime entitete

Deklaracija arhitekture

Telo arhitekture

```
architecture Demo of Adder is  
begin  
end Demo;
```

Ime arhitekture

N. Zimic

11-11

Način zapisa


- Logičen pogoj se lahko zapiše na tri načine:
 - zaporedno
 - paralelno
 - strukturalno

N. Zimic

11-12

Primer primerjalnika

 - Kot primer za načine zapisa si bomo ogledali primerjalnik:
 - vstopajo dva krat po štiri spremenljivke (A_0, A_1, A_2, A_3 in B_0, B_1, B_2, B_3),
 - izhod je rezultat primerjave ($A=B$).



N. Zimic

11-13

Način zapisa (nad.)

- Ne glede na način zapisa ostaja skupni (navedba knjižnice in deklaracija entitete) del enak:

```
library ieee;
use ieee.std_logic_1164.all;

entity eqcomp4 is
    port (A, B : in std_logic_vector(3 downto 0);
          Equals : out std_logic);
end eqcomp4;
```

Vhodi so deklarirani kot
vektor

Izhod je samo eden

N. Zimic

11-14

Zaporedni načina zapisa

- Primer zaporednega načina zapisa:
 - koda je sicer zaporedno napisana, vendar se moramo vedno zavedati, da se koda prevede v logično enačbo!

```
architecture seq1 of eqcomp4 is
begin
  process(A, B)
  begin
    if A = B then
      Equals <= '1';
    else
      Equals <= '0';
    end if;
  end process;
end seq1;
```

N. Zimic

11-15

Zaporedni načina zapisa (nad.)

- Koda se ne izvaja zaporedno!!!
 - koda je sicer zaporedno napisana, vendar se moramo vedno zavedati, da se koda prevede v logično enačbo!

```
architecture seq2 of eqcomp4 is
begin
  process(A, B)
  begin
    Equals <= '0';
    if A = B then
      Equals <= '1';
    end if;
  end process;
end seq2;
```

N. Zimic

11-16

Paralelni način zapisa

- V tem načinu vezje opišemo z logičnimi enačbami:


```
architecture concurrent_bool of eqcomp4 is
begin
    Equals <= not(A(0) xor B(0)) and
              not(A(1) xor B(1)) and
              not(A(2) xor B(2)) and
              not(A(3) xor B(3));
end concurrent_bool;
```

```
architecture concurrent of eqcomp4 is
begin
    Equals <= '1' when (A = B) else '0';
end concurrent;
```

N. Zimic

11-17

Strukturalni način zapisa

 

N. Zimic

11-18

Strukturalni način zapisa (nad.)

- V tem načinu povezujemo gradnike med seboj.

Gradnik je lahko definiran posebej ali pa v knjižnici

```
architecture structure of eqcomp4 is
  signal X : std_logic_vector(3 downto 0);
begin
  u0 : xnor2 port map
    (A => A(0), B => B(0), O => X(0));
  u1 : xnor2 port map
    (A => A(1), B => B(1), O => X(1));
  u2 : xnor2 port map
    (A => A(2), B => B(2), O => X(2));
  u3 : xnor2 port map
    (A => A(3), B => B(3), O => X(3));
  u4 : and4 port map
    (A => X(0), B => X(2), C => X(3),
     D => X(4), O => Equals);
end structure;
```

N. Zimic

11-19

Primer realizacije

- Primer realizacije preklopne funkcije:

$$Y = AB \vee CD$$

- Realizacija konjunkcije in disjunkcije:

```
entity And2 is
  port (A, B : in bit;
        Y : out bit);
end And2;

architecture Gate of And2 is
begin
  Y <= A and B;
end Gate;
```

```
entity Or2 is
  port (A, B : in bit;
        Y : out bit);
end Or2;

architecture Gate of Or2 is
begin
  Y <= A or B;
end Gate;
```

N. Zimic

11-20

```

entity AndOr is
  port ( A, B, C, D : in bit;
         Y : out bit);
end AndOr;

architecture struct of AndOr is
component Or2
  port ( A, B : in bit;
         Y : out bit);
end component;

component And2
  port ( A, B : in bit;
         Y : out bit);
end component;

signal A1, B1 : bit;

begin
  U1: And2 port map
    ( A => A, B => B, Y => A1);
  U2: And2 port map
    ( A => C, B => D, Y => B1);
  U3: Or2 port map
    ( A => A1, B => B1, Y => Y);
end struct;

```

N. Zimic 11-21

The diagram shows the VHDL code structure with four red curly braces on the right side:

- A brace above the first two lines of the entity declaration: **Deklaracija entitete**
- A brace above the two component declarations: **Deklaracija uporabljenih entitet**
- A brace above the signal declaration: **Signali**
- A brace above the three port map statements: **Povezovanje uporabljenih entitet**

Primer realizacije (nad.)

- Krajši način zapisa:

```

entity AndOr is
  port ( A, B, C, D : in bit;
         Y : out bit);
end AndOr;

architecture struct of AndOr is
  signal A1, B1 : bit;

begin
  U1: entity work.And2(gate)
    port map( A => A, B => B, Y => A1);
  U2: entity work.And2(gate)
    port map( A => C, B => D, Y => B1);
  U3: entity work.And2(gate)
    port map( A => A1, B => B1, Y => Y);
end struct;

```

N. Zimic 11-22

Primer realizacije (nad.)

- Enostavne logične operatorje lahko zapišemo v obliki enačbe:

```
entity AndOr is
    port ( A, B, C, D : in bit;
           Y : out bit);
end AndOr;


architecture struct of AndOr is
begin
    Y <= (A and B) or (C and D);
end struct;
```

N. Zimic

11-23

Dekodirnik

- Primer dekodirnika

 

N. Zimic

11-24

Dekodirnik (nad.)

```
library ieee;
use ieee.std_logic_1164.all;
use IEEE.std_logic_arith.all;
entity Decoder is
    port (X: in std_logic_vector (1 downto 0);
          m: out std_logic_vector (3 downto 0);
end Decoder;


architecture struct of Decoder is
begin
    m <= "0001" when X="00" else
    "0010" when X="01" else
    "0100" when X="10" else
    "1000";
end struct;
```

N. Zimic

11-25

Multiplekser

 - Primer multiplekserja z dvema naslovnima vhodoma



N. Zimic

11-26

Multiplekser (nad.)

```
library ieee;
use ieee.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity mux_gate is
    port (X: in std_logic_vector (1 downto 0);
          K0,K1,K2,K3: in std_logic;
          Y: out std_logic);
end mux_gate;

architecture struct of mux_gate is

begin
    Y <= K0 when X="00" else
        K1 when X="01" else
        K2 when X="10" else
        K3;
end struct;
```

N. Zimic

11-27

Postavitev generičnih tipov

- Generične tipe se uporablja pri postavitvi struktur, pri katerih se natančna velikost parametrov določi pri prenosu.
- Strukture so lahko postavljene neodvisno od velikosti parametrov
 - primer takšne strukture je lahko vsota dveh besed, pri čemer dolžina besede ni določena,
 - dolžina se pred implementacijo določi na višjem nivoju in se prenese preko parametrov

N. Zimic

11-28

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity Adder is
  generic (
    Width : integer range 2 to 32 := 16);
  port (
    A, B : in unsigned(Width-1 downto 0);
    Y : out unsigned(Width-1 downto 0));
end Adder;

architecture RTL of Adder is
begin
  Y <= A + B;
end RTL

```

```

Adder_1: Adder
generic map (Width => 22)
port map (A => A, B => B, Y => Y);

```

N. Zimic

11-29


Zakasnitve v vezjih

- Časovni parametri se uporabljajo samo za preverjanje pravilnosti delovanja v času simulacije,
- Signali, krajši od zakasnitve, se na izhodu ne pojavijo!
- Krajši signali se pojavijo samo pri uporabi ukaza “transport”

N. Zimic

11-30
 
```
X <= '0', '1' after 1 ns, '0' after 3 ns, '1' after 8 ns, '0' after 13 ns;  
Y <= X after 4 ns;
```



N. Zimic

11-31

Zakasnitve v vezjih (nad.)


- Zakasnitev v vezjih ni možno določiti nad strukturami, ki se pred realizacijo v vezjih še spremenijo (minimizirajo)
- V spodnjem primeru zakasnitve ni možno izračunati:

```
Y <= ((A and B) or (C and D)) after 4 ns;
```


N. Zimic

11-32


Model brez zakasnitve

 

Brez zakasnitve

 


Z zakasnitvijo

 

N. Zimic

11-33

Paralelna izvedba

 

N. Zimic

11-34

```

library ieee;
use ieee.std_logic_1164.all;

entity Test is
    port (A, B : in std_logic;
          X, Y : out std_logic);
end Test;


architecture Concurrent of Test is
begin
    X <= A xor B;
    with A select Y <= B when '1',
                     'Z' when '0',
                     '-' when others;
end Concurrent;

```

N. Zimic

11-35

Notranji signali

 

N. Zimic

11-36

```

library ieee;
use ieee.std_logic_1164.all;

entity Test is
  port (A, B : in std_logic;
        X, Y : out std_logic);
end Test;

architecture Internal of Test is

  signal Int : std_logic;


begin
  Int <= A xor B;
  X <= not Int ;
  Y <= Int and A;
end Internal;

```

N. Zimic

11-37

Zaporedni stavki (procesi)

 

N. Zimic

11-38

```

library ieee;
use ieee.std_logic_1164.all;

entity Test is
    port (A, B : in std_logic;
          X, Y : out std_logic);
end Test;


architecture Proc of Test is
begin
    P1: process (A, B)
        -- postavitev signalov ni dovoljena
        begin
            if A = '1' and B = '0' then
                X <= A;
                Y <= '1';
            else
                X <= B;
                Y <= '0';
            end if;
        end process P1;
    end Proc;

```

N. Zimic

11-39

Zaporedni stavki (procesi)

 

N. Zimic

11-40

```

library ieee;
use ieee.std_logic_1164.all;
entity Test is
    port(A, B : in std_logic;
         X, Y : out std_logic);
end Test;

architecture Proc of Test is
    signal Internal : std_logic;

begin
    P1 : process (A, B)
    begin
        if A = '1' and B = '0' then
            X <= A; Internal <= '0';
        else
            X <= B; Internal <= '1';
        end if;
    end process P1;

    P2 : process (A, B, Internal)
    begin
        if Internal = '1' then
            Y <= A;
        else
            Y <= B;
        end if;
    end process P2;
end Proc;

```

Procesa se med simulacijo
izvajata paralelno!

N. Zimic


11-41

Primerjava zaporednih in paralelnih stavkov

```

architecture Concurrent of Test is
begin
    Y <= A or B;
    Y <= C and D;
end Concurrent;

```

 


Prevajalnik javi napako

```

architecture Sequential of Test is
begin
    process(A, B, C, D)
    begin
        Y <= A or B;
        Y <= C and D;
    end process;
end Sequential;

```

 

Prevajalnik upošteva
zadnji izraz

N. Zimic

11-42

Simulacija

- Simulacija se izvaja na osnovi dogodkov (sprememb vrednosti signalov).
- Pri vsaki spremembi signala se izračuna nova vrednost preklopne funkcije.
- Izračun se ponavlja dokler ni več nobene spremembe signalov v vezju.
- Ko ni več sprememb, se realen čas pomakne na naslednjo spremembo na vhodu.


N. Zimic

11-43

Primer simulacije


```
architecture sim of Test is
    signal A, B, C, D : std_logic := '0';
    signal S1, S2, Y : std_logic;

 begin
    A <= '0' after 5 ns, '1' after 10 ns;
    B <= '1' after 5 ns;
    C <= '0' after 5 ns, '1' after 10 ns;
    D <= '1' after 5 ns;
    S1 <= A xor B;
    S2 <= C xor D;
    Y <= S1 and S2;
end Sim;
```



N. Zimic

11-44

 

N. Zimic

11-45

Definicija konstant

- Poljubnemu podatkovnemu tipu lahko priredimo ustrezno konstantno vrednost.
- Primer postavitve konstant:

```
constant Mult : std_logic_vector := "0001"; -- Opcode multiply
constant Width : integer := 12;
```

N. Zimic

11-46

Signali

- Signale si lahko predstavljamo kot povezave med elementi.
- Signali lahko predstavljajo tudi pomnilne celice.

```
signal shiftReg : std_logic_vector(7 downto 0);  
shiftreg <= shiftreg(6 downto 0) & Input;
```

- Signalom se lahko priredi začetna vrednost, vendar ta običajno ne vpliva na sintezo vezja.

```
signal Count : std_logic_vector(3 downto 0) := "0101";
```

N. Zimic

11-47

Spremenljivke

- Spremenljivke se uporabljajo samo v procesih in podprogramih.

```
architecture will_work of my_and is  
begin  
adding: process (a_bus)  
variable tmp: bit;  
begin  
tmp := '1';  
for i in 7 downto 0 loop  
tmp := a_bus(i) and tmp;  
end loop;  
x <= tmp;  
end process;  
end will_work;
```

N. Zimic

11-48

Primeri podatkovnih tipov

Števni tipi

```
type MyBit is ('0', '1');
type Barva is (Zelena, Rumena, Modra, Bela);
```

Celoštevilčni tipi – privzeta dolžina je 32 bitov

```
type Count is integer range 0 to 10;
```

Polja

```
type MyBitVector is array (natural range <>) of Mybit;
type MyByte is array (natural range 7 downto 0) of Mybit;
```

N. Zimic

11-49

Zapis

```
type FloatType is record
    Sign : MyBit;
    Mantissa : MyBitVector(7 downto 0);
    Exponent : MyBitVector(15 downto 0);
end record;
```

Podtipi

```
subtype Byte is std_ulogic_vector 7 downto 0;
```

N. Zimic

11-50

Primeri standardnih tipov

```
package STANDARD is
    type boolean is (false, true);
    type bit is ('0', '1');
    type character is ( ASCII chars... );
    type severity_level is (note, warning, error, failure);
    type integer is range -2147483648 to 2147483647;
    type real is range -1.0E308 to 1.0E308;
    type time is range -2147483647 to 2147483647
        units
            fs;
            ps = 1000 fs;
            ns = 1000 ps;
            us = 1000 ns;
            ms = 1000 us;
            sec = 1000 ms;
            min = 60 sec;
            hr = 60 min;
        end units;
    ...

```

N. Zimic

11-51

```
...
subtype delay_length is time range 0 fs to time'high;
impure function now return delay_length;
subtype natural is integer range 0 to integer'high;
subtype positive is integer range 1 to integer'high;
type string is array (positive range <>) of character;
type bit_vector is array (natural range <>) of bit;
type file_open_kind is (
    read_mode,
    write_mode,
    append_mode);
type file_open_status is (
    open_ok,
    status_error,
    name_error,
    mode_error);
attribute foreign : string;
end STANDARD;
```

N. Zimic

11-52

Atributi

- Primer atributov, ki so definirani v jeziku VHDL:

```
clock'event vrne true pri spremembi vrednosti ure  
  
signal A : unsigned(3 downto 0)  
  
A'left vrne 3  
A'right vrne 0  
A'range vrne 3 downto 0  
A'length vrne 4
```

N. Zimic

11-53

Tipi paketa std_logic_1164

Tip bit je definiran:
type bit **is** ('0', '1');

Tip std_ulogic v paketu std_logic_1164 je definiran:
type std_ulogic **is** ('U', -- Uninitialized
 'X', -- Forcing Unknown
 '0', -- Forcing 0
 '1', -- Forcing 1
 'Z', -- High Impedance
 'W', -- Weak Unknown
 'L', -- Weak 0
 'H', -- Weak 1
 '-' -- Don't care
);

Vektor std_ulogic_vector je definiran:
type std_ulogic_vector **is array** (natural range <>) **of** std_ulogic;


N. Zimic

11-54

Pravilnostna tabela std_logic

- Pri povezanih izhodih, je potrebno upoštevati razširjeno pravilnostno tabelo.

	U	X	0	1	Z	W	L	H	-
U	U	U	U	U	U	U	U	U	U
X	U	X	X	X	X	X	X	X	X
0	U	X	0	X	0	0	0	0	X
1	U	X	X	1	1	1	1	1	X
Z	U	X	0	1	Z	W	L	H	X
W	U	X	0	1	W	W	W	W	X
L	U	X	0	1	L	W	L	W	X
H	U	X	0	1	H	W	W	H	X
-	U	X	X	X	X	X	X	X	X

 

N. Zimic

11-55

Funkcije paketa std_logic_1164

Logične funkcije:

`and, nand, or, xor, xnor, not`

Funkcije za pretvorbo tipov:

`To_bit, To_bitvector, To_StdULogic,
To_StdULogicVector, ToStdLogicVector`

Funkcije za določanje fronte:

`rising_edge() and falling_edge()`

Paket std_logic_1164 ne vsebuje aritmetičnih funkcij!

N. Zimic

11-56

Paket numeric_std

- V paketu numeric_std so postavljeni numerični tipi:

```
type unsigned is array (natural range <>) of std_logic;
type signed is array (natural range <>) of std_logic;
```

- V paketu numeric_std so postavljene numerične funkcije in funkcije za pretvorbo tipov.

N. Zimic

11-57

Primeri pretvorbe

```
architecture Y of X is
    signal S : std_logic_vector(7 downto 0);
    signal A, B : unsigned(7 downto 0);
    signal MyInt : integer;
begin
    S <= B; -- prevajalnik javi napako

    S <= std_logic_vector(A); -- pravilna pretvorba tipa

    S <= std_logic_vector(A + B); -- vsota je definirana v paketu

    MyInt <= to_integer(A + B); -- pretvorba v integer

    A <= unsigned(S) + MyInt; -- napačni tipi
end Y;
```

N. Zimic

11-58

Pranje poljem

```
architecture assign of Examples is
    signal Byte : std_logic_vector(7 downto 0) := "01010101";
    signal Word : std_logic_vector(15 downto 0);

begin
    Byte <= "00001111";
    Byte <= ('1', '0', '1', '0', '1', '0', '1', '0');
    Byte <= X"0F";
    Byte <= (others => '1');
    Byte <= (7 | 6 => '1', others => '0');
    Byte <= (7 => '1', 4 => '1', 3 downto 1 => '0', others => '0');
    Word <= X"FF" & Byte;
    Word(15 downto 8) <= (others => Byte(7));
    Word(7 downto 0) <= Byte;
end Examples;
```

N. Zimic

11-59

Stavek wait

```
process -- Tvorba signala za reset
begin
    Reset <= '0';
    wait for 15 ns;
    Reset <= '1';
    wait;
end process;
```

```
process -- Tvorba kratkega impulza
begin
    Spare_n <= '1';
    wait for 200 ns;
    Spare_n <= '0';
    wait for 8 ms;
    Spare_n <= '1';
    wait;
end process;
```

N. Zimic

11-60

```

process -- Tvorba urinega impulza
begin
    Clk <= '0';
    wait for 10 ns;
    Clk <= '1';
    wait for 10 ns;
end process;

```

```

process -- Čakaj, da se urin impulz spremeni na 0
begin
    wait until Clk = '0';
    A <= Stimulus;
end process

```

```

process -- Čakaj na spremembo signalov A, B ali C
begin
    wait on A, B, C;
    X <= A and b and C;
end process;

```

N. Zimic

11-61

Stavek if

```

if Count = 1 then
    OutPut <= '1';
else
    OutPut <= '0';
end if;

```

```

if Count = 1 then
    A := 10;
elsif State = Idle then
    A := 20;
else
    A := 30;
end if;

```

N. Zimic

11-62

Stavek case

```
case PresentState is
    when Idle =>
        Output <= '1';
        NexState <= S1;
    when S1 =>
        Output <= '0';
        NexState <= S2;
    when S2 =>
        Output <= '1';
        NexState <= S1;
end case;
```

N. Zimic

11-63

```
case OPCode is
    when "0000" | "0001" | "0010" | "0011" =>
        Result <= A;
    when "1000" | "1001" | "1010" | "1011" | "1100" | "1101" | "1110" | "1111" =>
        Result <= B;
    when "0100" | "0101" =>
        Result <= C;
    when others => -- All possible cases must be covered
        null; -- do nothing
end case;
```

N. Zimic

11-64

Stavki loop, next, exit

```
A := 0;
for i in 0 to 10 loop
    A := A + B(i);
end loop;
```

```
for i in 0 to 10 loop
    next when i = 1; -- preskoči ukaze pri izpolnjenem pogoju
    A := A + B(i);
end loop;
```

```
while A > B loop
    B := B * 2;
end loop;
```

N. Zimic

11-65

```
i := 0;
loop
    i := i + 1;
    exit when i = 10;
end loop;
```

```
L1 : for i in 10 downto 0 loop
    L2 : loop
        next L1 when Done = '1'; -- pri izpolnjenem pogoju L1
    end loop L2;
end loop L1;
```

N. Zimic

11-66

Stavki with, select, when

```
with selection_signal select
    signal_name <= value_a when value_1_of_selection_signal,
                            value_b when value_2_of_selection_signal,
                            value_c when value_3_of_selection_signal,
                            value_x when last_value_of_selection_signal;


-- če niso naštete vse možnosti, mora biti zadnja others
```

N. Zimic

11-67

Stavka when, else
 
```
signal_name <= value_a when condition_1 else,
                            value_b when condition_2 else,
                            value_c when condition_3 else,
                            value_x;
```



```
Y <= a when (s = "00") else,
           b when (s = "01") else,
           c when (s = "10") else,
           d;
```

N. Zimic


11-68

Pomnilna celica - latch

```
library ieee;
use ieee.std_logic_1164.all;

entity Latches is
  port (
    A, En : in std_logic;
    X : out std_logic);
end Latches;

 architecture RTL of Latches is
begin
  P1 : process(En, A)
  begin
    if En = '1' then
      X <= A;
    end if;
  end process;
end RTL;
```



N. Zimic


11-69

D- pomnilna celica

```
library ieee;
use ieee.std_logic_1164.all;

entity Latches is
  port (
    D, Clk : in std_logic;
    Q : out std_logic);
end Latches;

 architecture RTL of Latches is
begin
  P1 : process(Clk)
  begin
    if Clk = '1' and Clk'event then
      Q <= D;
    end if;
  end process;
end RTL;
```



N. Zimic

11-70

D- pomnilna celica z vhodom reset

```



ASynch : process(Clk, Reset)
begin
  if Reset = '1' then
    Q1 <= '0';
  elsif rising_edge(Clk) then
    Q1 <= D1;
  end if;
end process;

```

```

Synch : process(Clk)
begin
  if rising_edge(Clk) then
    if Reset = '1' then
      Q2 <= '0';
    else
      Q2 <= D2;
    end if;
  end if;
end process;

```

  

N. Zimic

11-71

8-bitni števec

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity Counter is
  port(Clk, Reset, Enable : in std_logic;
       Count : out unsigned(7 downto 0));
end Counter;
architecture RTL of Counter is
begin
  Cnt : process(Clk, Reset)
    variable CountReg : unsigned(7 downto 0);
  begin
    if Reset = '1' then
      CountReg := (others => '0');
    elsif rising_edge(Clk) then
      if Enable = '1' then
        CountReg := CountReg + 1;
      end if;
    end if;
    Count <= CountReg;
  end process Cnt;
end RTL;

```

N. Zimic

11-72

Procedure in funkcije

- Funkcija ima, za razliko od procedure, samo en izhod.
- Pri postavljanju funkcij in procedur je potrebno upoštevati, da se bodo te prevedla v obliko, ki bo primerna za zapis v integrirano vezje.
- Postavijo se lahko različne funkcije z enakim imenom, ki pa se razlikujejo po tipu parametrov (*Overloading operators*).

N. Zimic

11-73

```
library ieee;
use ieee.std_logic_1164.all;

package smd098_pkg is
    function OR_reduce (A : std_logic_vector)
        return std_logic;
end smd098_pkg;

package body smd098_pkg is
    function OR_reduce (A : std_logic_vector)
        return std_logic is

        variable temp : std_logic;

    begin
        temp := '0';
        L1: for i in A'range loop
            temp := temp or A(i);
        end loop L1;
        return temp;
    end function OR_reduce;
end smd098_pkg;
```

N. Zimic

11-74

```

library ieee;
use ieee.std_logic_1164.all;
use work.smd098_pkg.all;

entity test_or is
    port (A : in std_logic_vector(3 downto 0);
          Y1, Y2 : out std_logic);
end test_or;

architecture RTL of test_or is
begin
    -- Concurrent fun. call
    Y1 <= OR_reduce(A);
    process(A)
    begin
        -- Sequential fun. call
        Y2 <= OR_reduce(A);
    end process;
end RTL;

```

N. Zimic

11-75

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

package smd098_pkg is
    function OR_reduce (A : std_logic_vector) return std_logic;
    function OR_reduce (A : unsigned) return std_logic;
end smd098_pkg;

package body smd098_pkg is
    function OR_reduce (A : std_logic_vector) return std_logic is
        variable temp : std_logic;
    begin
        temp := '0';
        L1 : for i in A'range loop
            temp := temp or A(i);
        end loop L1;
        return temp;
    end function OR_reduce;

    function OR_reduce (A : unsigned) return std_logic is
        variable temp : std_logic;
    begin
        temp := '0';
        L1 : for i in A'range loop
            temp := temp or A(i);
        end loop L1;
        return temp;
    end function OR_reduce;
end smd098_pkg;

```

N. Zimic

11-76

```

package smd098_pkg is

    procedure DFF (signal Clk : in std_logic;
                  signal D : in std_logic_vector;
                  signal Q : out std_logic_vector);
end smd098_pkg;

package body smd098_pkg is
    procedure DFF (signal Clk : in std_logic;
                  signal D : in std_logic_vector;
                  signal Q : out std_logic_vector) is
        begin
            if rising_edge(Clk) then
                Q <= D;
            end if;
        end procedure DFF;
end smd098_pkg;

```

N. Zimic

11-77

```

library ieee;
use ieee.std_logic_1164.all;
use work.smd098_pkg.all;

entity test_DFF is
    port (Clk : in std_logic;
          A : in std_logic_vector(3 downto 0);
          Y1, Y2, Y3 : out std_logic_vector(3 downto 0));
end test_DFF;

architecture RTL of test_DFF is
begin
    -- Concurrent proc. call
    DFF(Clk => Clk, D => A, Q => Y1);
    -- Concurrent proc. call, positional association
    DFF(Clk, A, Y2);
    -- Sequential procedure call
    process(Clk)
    begin
        DFF(Clk, A, Y3);
    end process;
end RTL;

```

N. Zimic

11-78

Knjižnice

- V knjižnicah lahko postavimo:
 - definicije tipov,
 - deklaracija konstant,
 - funkcije in procedure,
 - komponente.
- Primer vključevanja knjižnice:

```
library mylib;
use mylib.mypackage.all;
```

Knjižnica Zbirka Element


```
library mylib;
use mylib.mypackage.myfunc;
```

N. Zimic

11-79

Sekvenčna vezja

 
- Sekvenčno vezje je sestavljeno iz kombinatornega dela in pomnilnih celic:



N. Zimic

11-80

Primer avtomata

 

Izhodna funkcija

State	oe	we
idle	0	0
decision	0	0
write	0	1
read	1	0

N. Zimic

11-81

```

entity example is port (
    read_write, ready, clk : in bit;
    oe, we : out bit);
end example;

architecture state_machine of example is
    type StateType is (idle, decision, read, write);
    signal present_state, next_state : StateType;
begin
state_comb:process(present_state, read_write, ready) begin
    case present_state is
        when idle => oe <= '0'; we <= '0';
        if ready = '1' then
            next_state <= decision;
        else
            next_state <= idle;
        end if;
        when decision => oe <= '0'; we <= '0';
        if (read_write = '1') then
            next_state <= read;
        else
            next_state <= write;
        end if;
    ...
  
```

N. Zimic

11-82

```

...
when read =>                               oe <= '1'; we <= '0';
    if (ready = '1') then
        next_state <= idle;
    else
        next_state <= read;
    end if;
when write =>                             oe <= '0'; we <= '1';
    if (ready = '1') then
        next_state <= idle;
    else
        next_state <= write;
    end if;
end case;
end process state_comb;

state_clocked:process(clk) begin
    if (clk'event and clk='1') then
        present_state <= next_state;
    end if;
end process state_clocked;

end architecture state_machine; --"architecture" is optional; for clarity

```